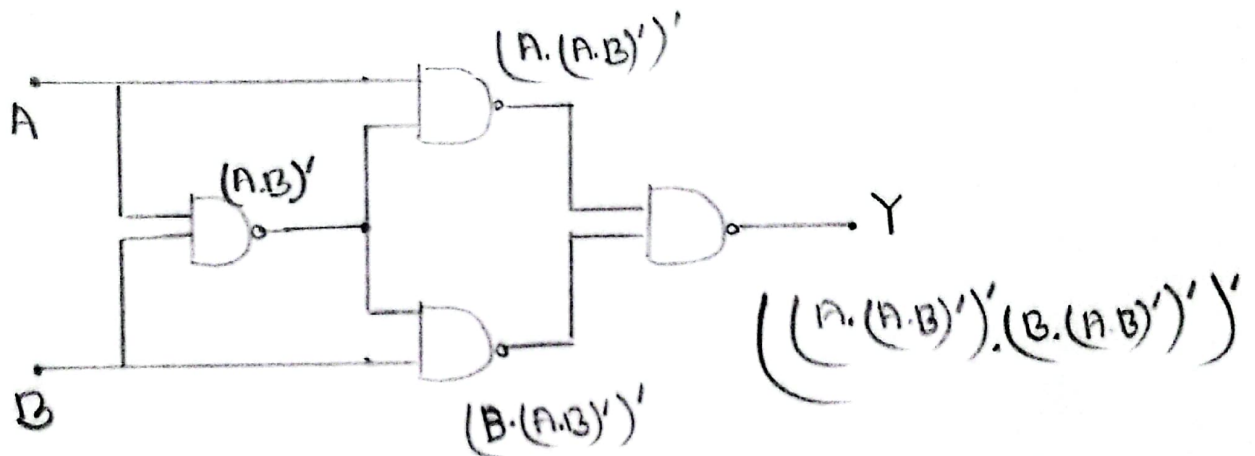


Experiment name : Applications of Boolean Algebra

Required components and equipment:

- Breadboard
- ~~Come~~
- Connecting wires
- IC 7400 (NAND Gate)

Experimental Setup:



Results and Discussions:

Here the Boolean equation for the output is $((A.(A.B)')' . (B.(A.B)')')'$. Using some boolean algebra properties we can easily simplify the equation and find the output.

Now, $((A.(AB)')') . (B.(AB)')')'$

$$= ((A.(AB)')')' + ((B.(AB)')')' \quad [\text{De Morgan Theorem}]$$

$$= A(AB)' + B(AB)' \quad [\because (A')' = A]$$

$$= A(A' + B') + B(A' + B') \quad [\text{De Morgan Theorem}]$$

$$= AA' + AB' + BA' + BB'$$

$$= 0 + AB' + BA' + 0 \quad [\because A.A' = 0]$$

$$= AB' + BA'$$

A	B	A'	B'	A'B	AB'	A'B+AB'
0	0	1	1	0	0	0
0	1	1	0	1	0	1
1	0	0	1	0	1	1
1	1	0	0	0	0	0

Truth Table

$A \oplus B$
0
1
1
0

Truth Table of XOR Gate

The Boolean equation for this output is

$Y = (A.(AB)')' . (B.(AB)')'$. After simplifying the boolean equation we get $(AB' + BA')$. The circuit's function is identical to a single gate which is XOR Gate.