


## Objective :

- To get familiarized with fundamental logic gates and demonstrate the input output relationship of 2-input AND (IC - 7408), OR (IC - 7432) and NOT (IC - 7404) gates by constructing their truth tables.
- To get familiarized with other logic gates like NAND (IC - 7400), NOR (IC - 7402), XOR (IC - 7486) and XNOR (IC - 74266)


## Required Components and Equipment:

- Breadboard
- Connecting wires
- IC 7400, IC 7408, IC - 7432, ~~IC - 7406~~, IC 7404, IC 7402, IC - 7486, IC - 74266

## Experimental Setup:

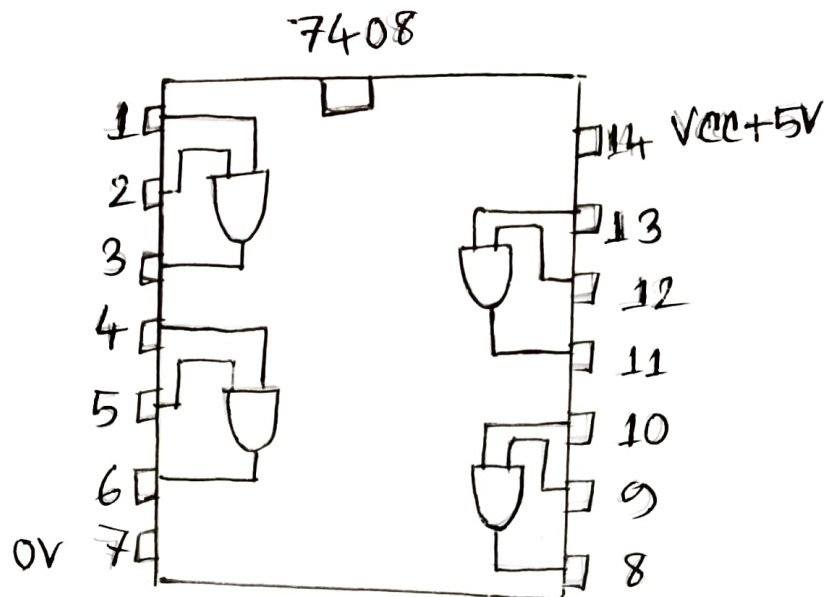

Pin layout of 7408  
figure: AND gate.

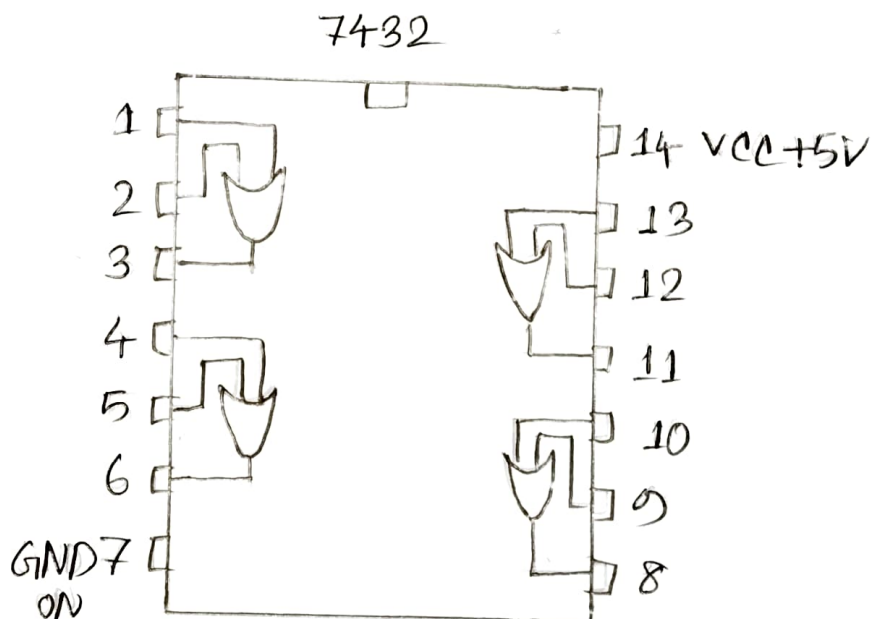

Pin layout of 7432  
figure: OR gate.

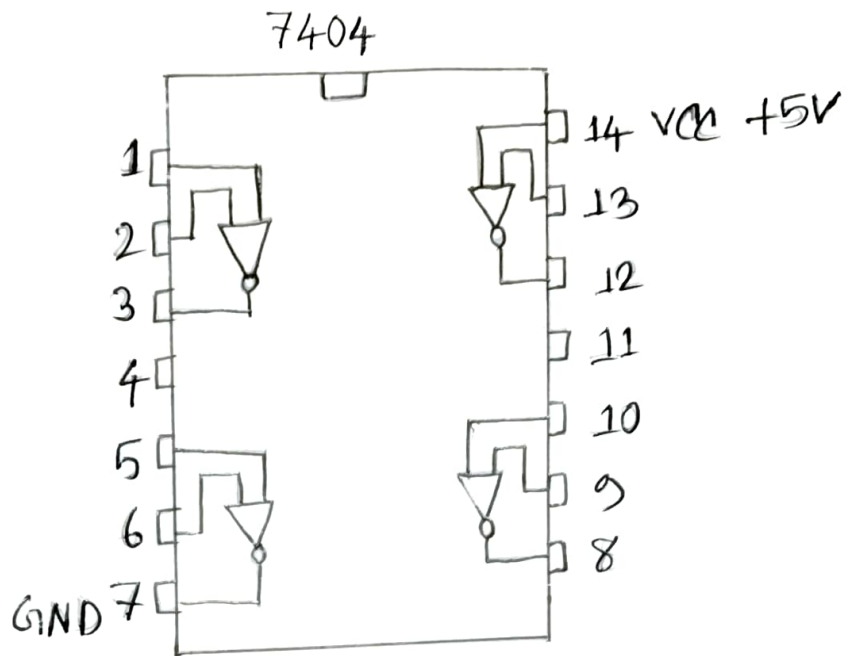


figure : NOT Gate

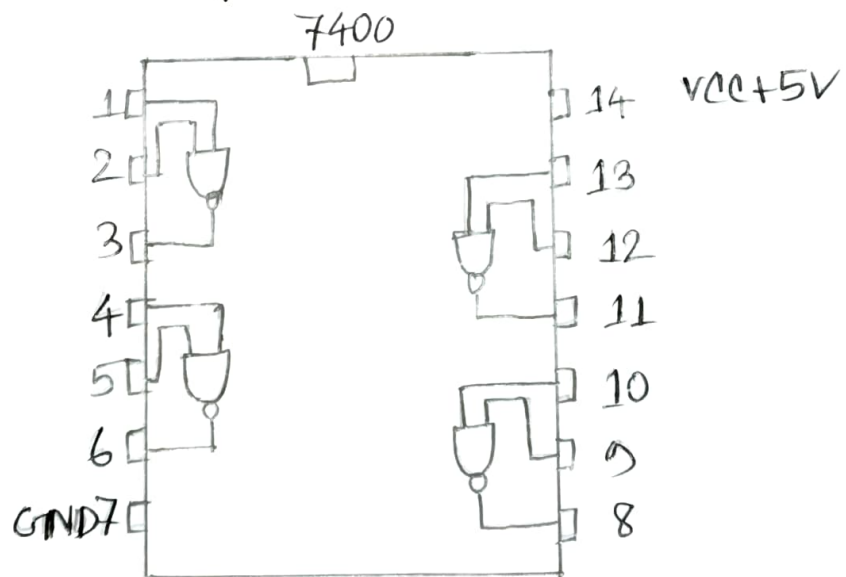


figure : NAND Gate.

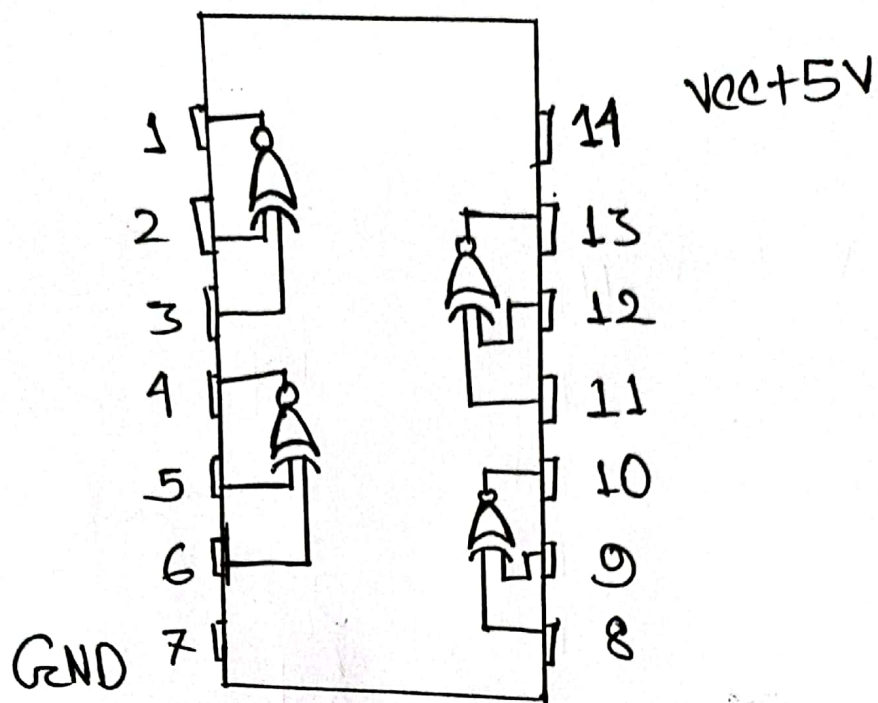


fig: NOR gate; Pin layout of 7402

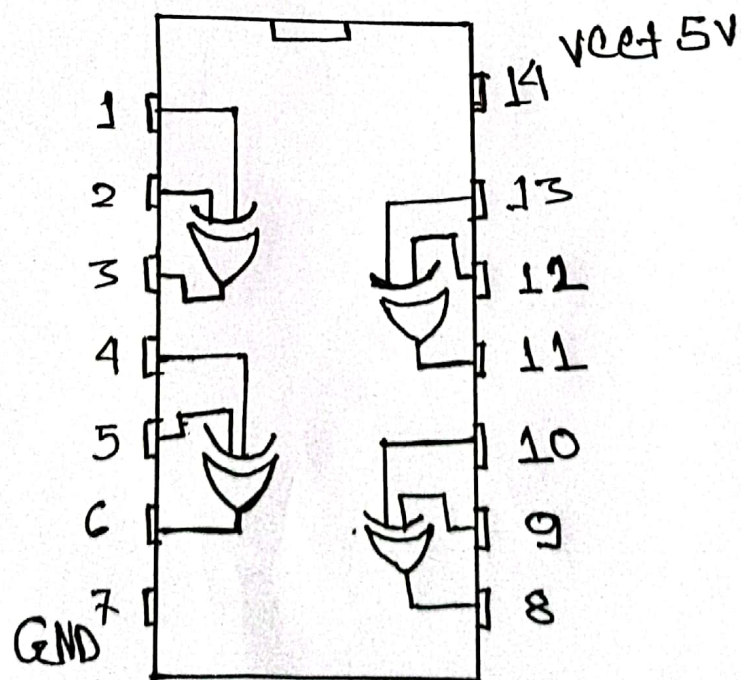


fig: XOR gate, pin layout of 7486.



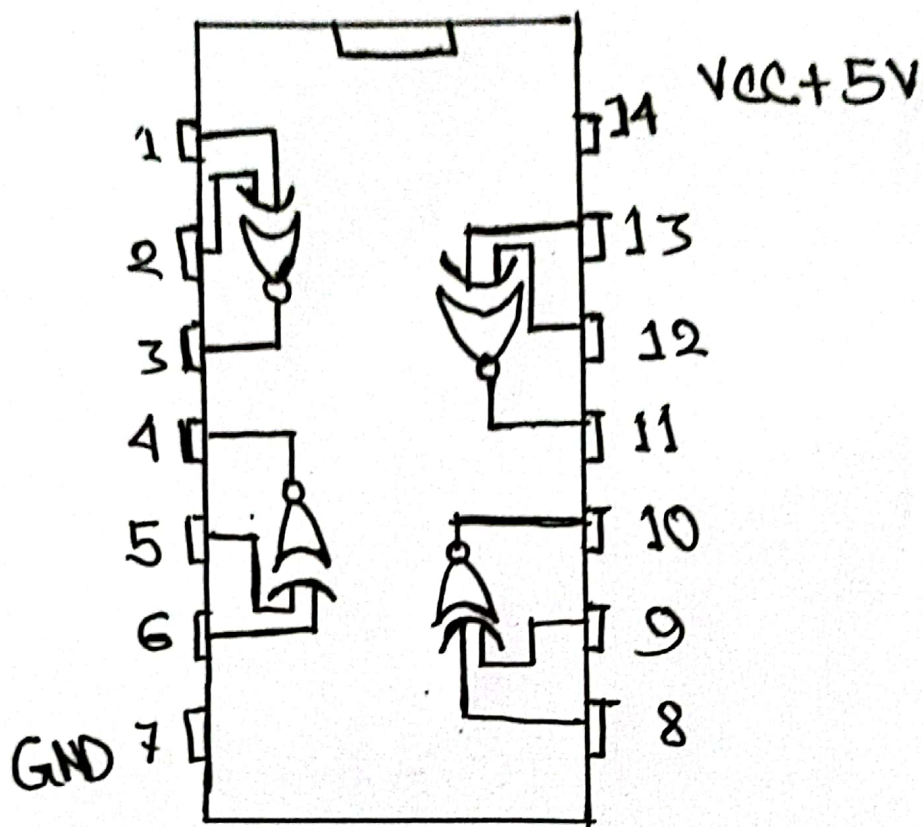


Fig: X-NOR Gate, pin layout of 74244

Results :

• Truth Table :

• AND Gate

Input		Output
A	B	
0	0	0
1	0	0
0	1	0
1	1	1

• OR Gate

Input		Output
A	B	
0	0	0
1	0	1
0	1	1
1	1	1

• NOT Gate

Input	Output
0	1
1	0

• NAND Gate

Input		Output
A	B	
0	0	1
1	0	1
0	1	1
1	1	0

• NOR Gate

Input		Output
A	B	
0	0	1
1	0	0
0	1	0
1	1	0

• XOR Gate

Input		Output
A	B	
0	0	0
1	0	1
0	1	1
1	1	0

• XNOR Gate

Input		Output
A	B	
0	0	1
1	0	0
0	1	0
1	1	1



## Discussion :

- Problem with some Faulty wires.
- Problem with some Faulty IC units.
- Every gate gives their output according to the truth table.