

## Name of the Experiment: Applications of Kmap method


- Objective :
- (i) To investigate the rules of kmap
  - (ii) To gain experience working with practical circuits
  - (iii) To simplify a complex function using kmap

### Required Components and Equipments:


- (i) Breadboard
- (ii) Connecting wires
- (iii) ~~AND, OR, NOT~~ AND, OR, NOT Gate

### Experimental Setup

#### (i) Function - 1

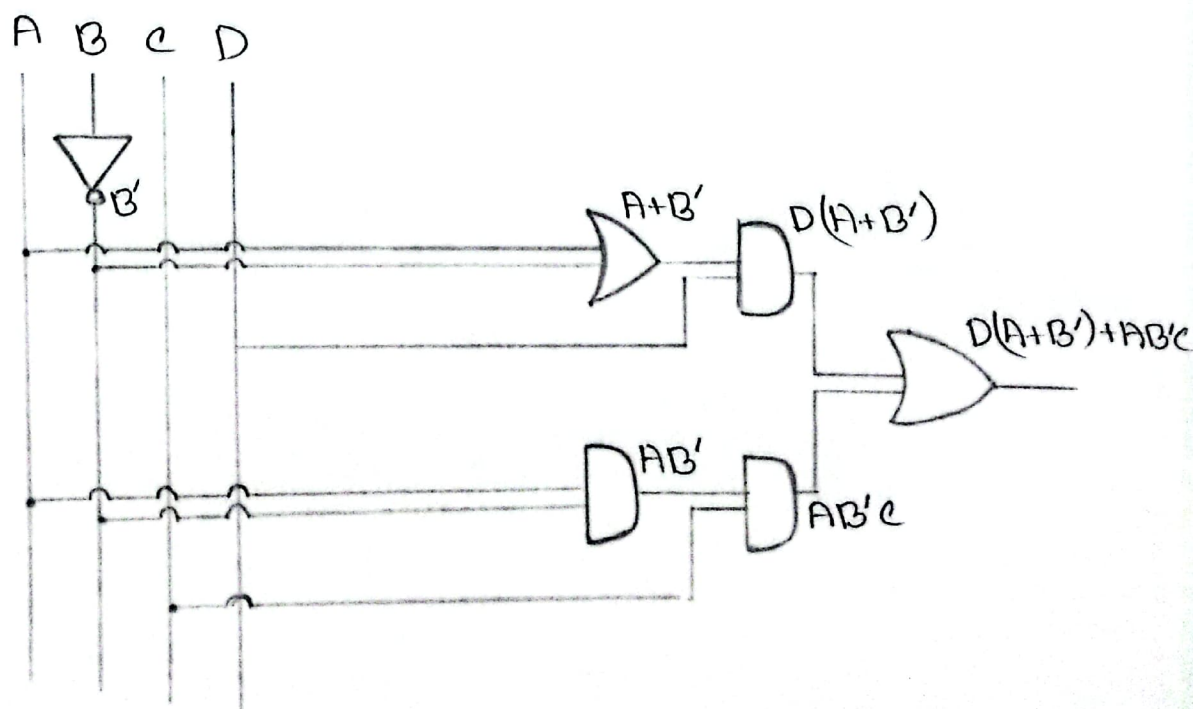

(ii) Function - 2

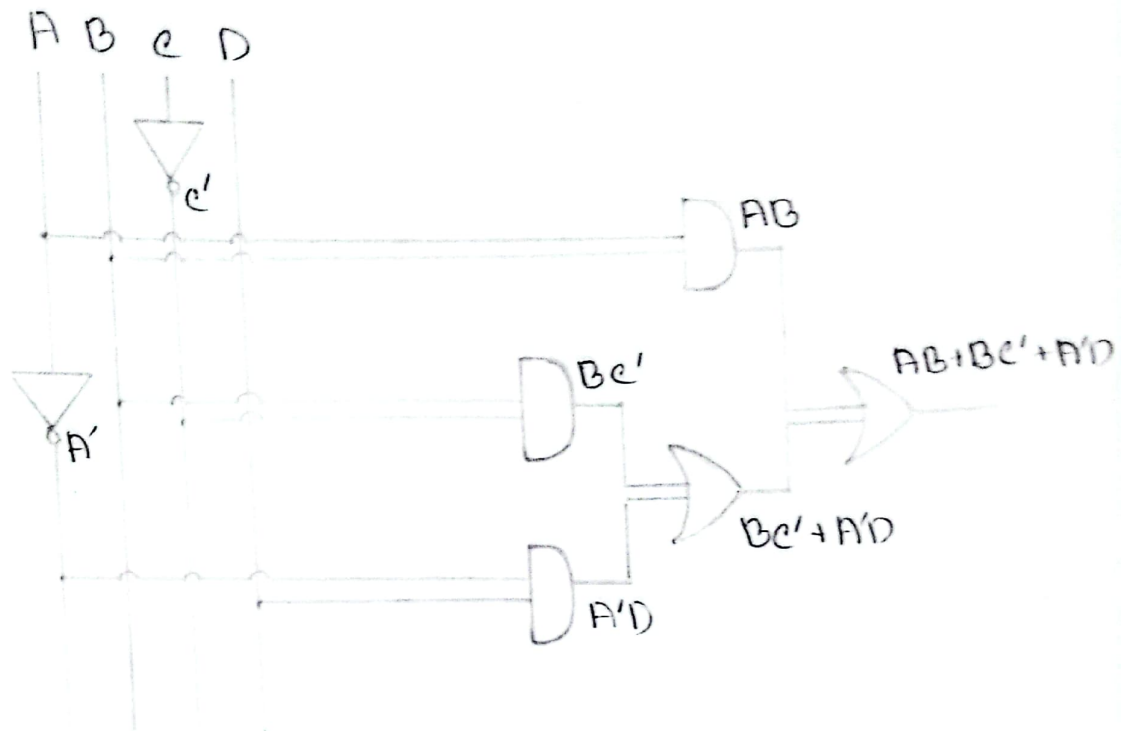

Results (K-Map) and Discussions :

(i) Function - 1

$$F(A, B, C, D) = \sum (1, 3, 9, 10, 11, 13, 15)$$

AB \ CD	C'D'	C'D	CD	CD'
A'B'	0	1	3	2
A'B	4	5	7	6
AB	12	13	15	14
AB'	8	9	11	10

$$F(A, B, C, D) = AD + B'D + AB'C = D(A + B') + AB'C$$

(ii) Function - 2

$$F(A, B, C, D) = \sum (1, 4, 15) + d(3, 5, 7, 12, 13, 14)$$

AB \ CD	C'D'	C'D	CD	CD'
A'B'	0	1	X	2
A'B	4	X	X	6
AB	X	X	1	X
AB'	8	9	11	10

$$F(A, B, C, D) = AB + BC' + A'D$$

Truth Table For Function - 1

	A	B	C	D	B'	A+B'	D(A+B')	AB'C	D(A+B')+AB'C
0	0	0	0	0	1	1	0	0	0
1	0	0	0	1	1	1	1	0	1
2	0	0	1	0	1	1	0	0	0
3	0	0	1	1	1	1	1	0	1
4	0	1	0	0	0	0	0	0	0
5	0	1	0	1	0	0	0	0	0
6	0	1	1	0	0	0	0	0	0
7	0	1	1	1	0	0	0	0	0
8	1	0	0	0	1	1	0	0	0
9	1	0	0	1	1	1	1	0	1
10	1	0	1	0	1	1	0	1	1
11	1	0	1	1	1	1	1	1	1
12	1	1	0	0	0	1	0	0	0
13	1	1	0	1	0	1	1	0	1
14	1	1	1	0	0	1	0	0	0
15	1	1	1	1	0	1	1	0	1

Truth Table for Function - 2

	A	B	C	D	A'	C'	AB	BC'	A'D	$AB + BC' + A'D$
0	0	0	0	0	1	1	0	0	0	0
1	0	0	0	1	1	1	0	0	1	1
2	0	0	1	0	1	0	0	0	0	0
3	0	0	1	1	1	0	0	0	1	1
4	0	1	0	0	1	1	0	1	0	1
5	0	1	0	1	1	1	0	1	1	1
6	0	1	1	0	1	0	0	0	0	0
7	0	1	1	1	1	0	0	0	1	1
8	1	0	0	0	0	1	0	0	0	0
9	1	0	0	1	0	1	0	0	0	0
10	1	0	1	0	0	0	0	0	0	0
11	1	0	1	1	0	0	0	0	0	0
12	1	1	0	0	0	1	1	1	0	1
13	1	1	0	1	0	1	1	1	0	1
14	1	1	1	0	0	0	1	0	0	1
15	1	1	1	1	0	0	1	0	0	1